

# GCSE OCR

Computer Science  
J277

1

## Logic diagrams and truth tables

Unit 8  
Logic and languages



PG ONLINE

# Objectives

- Construct truth tables for the following logic gates:
  - NOT
  - AND
  - OR
- Construct truth tables for simple logic circuits
- Interpret the results of truth tables
- Create, modify and interpret simple logic circuit diagrams

# Starter

- Consider a safe with two keys
- If both keys are used, the safe will open

```
if key1 AND key2 then  
    safeOpen = True
```

```
else  
    safeOpen = False
```

- What are the only possible values that key1 and key2 can be?
  - What values must they be to open the safe?



# Starter

Answers

```
if key1 AND key2 then
    safeOpen = True
else
    safeOpen = False
```

- What are the only possible values that key1 and key2 can be?
  - Key1 and key2 can only be True or False (lock or unlock)
- What values must they be to open the safe?
  - They must both be True to open the safe

# Binary situations

- Binary situations are common in daily life and can refer to things that can be in only one of two states:
  - Stop or Go
  - Pass or Fail
  - On or Off
- In computing terms
  - A binary 1 can represent True
  - A binary 0 can represent False



# Booleans in loops

- Booleans used in IF statements and loops

```
while doorOpen  
    turnOnLight()  
endwhile
```



# True or False?

Unlocking a smartphone:

- using a known fingerprint **or**
- using a correct PIN code?


```
if fingerprint OR correctPIN then  
    unlock = True
```

```
else  
    unlock = False
```


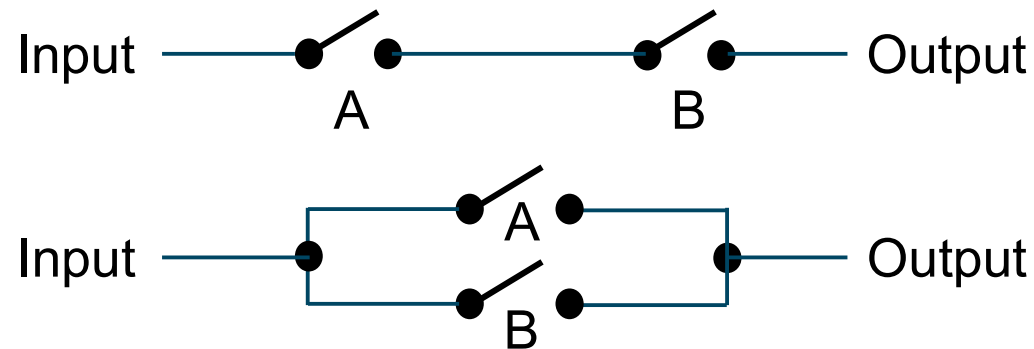
# Boolean functions

- AND, OR and NOT are Boolean operators
- A computer can calculate the results of **A AND B**, **A OR B**, or **NOT A**
  - What do these two circuit diagrams represent?





# Boolean functions


Answers

- What do these two circuit diagrams represent?



AND

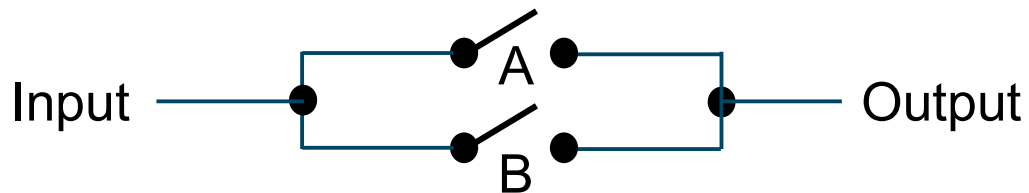Both switches must be down to complete the circuit



OR

Either switch needs to be down to complete the circuit

# Truth tables


- A **truth table** shows the output from all possible combinations of inputs from a Boolean expression
- If there are two inputs A AND B, there are four possible combinations of TRUE and FALSE
  - Both A and B must be True for the output to be True

Input A	Input B	A AND B
False	False	False
False	True	False
True	False	False
True	True	True

# Boolean function – AND

- It is also possible to use 1 and 0 to represent True and False
  - The below truth tables represent: IF a lift is on the correct floor **AND** the call button has been pressed THEN open the lift door
  - What are the values for *Open Life Door* and *P* below

Lift on correct floor	Button Pressed	Open Lift Door
False	False	?
False	True	?
True	False	?
True	True	?

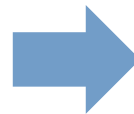

A	B	P
0	0	?
0	1	?
1	0	?
1	1	?




# Truth table – AND

Answers

- IF both inputs are **TRUE** then the output is **TRUE**

Lift on correct floor	Button Pressed	Open Lift Door
0	0	0
0	1	0
1	0	0
1	1	1

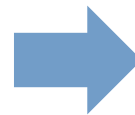


A	B	P
0	0	0
0	1	0
1	0	0
1	1	1




# Boolean function – OR

- IF lane1Open OR lane2Open
  - If lane one is open OR lane 2 is open then you can drive down the road
  - What is P?

lane1 Open	Lane2 Open	P
False	False	?
False	True	?
True	False	?
True	True	?

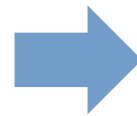

A	B	P
0	0	?
0	1	?
1	0	?
1	1	?

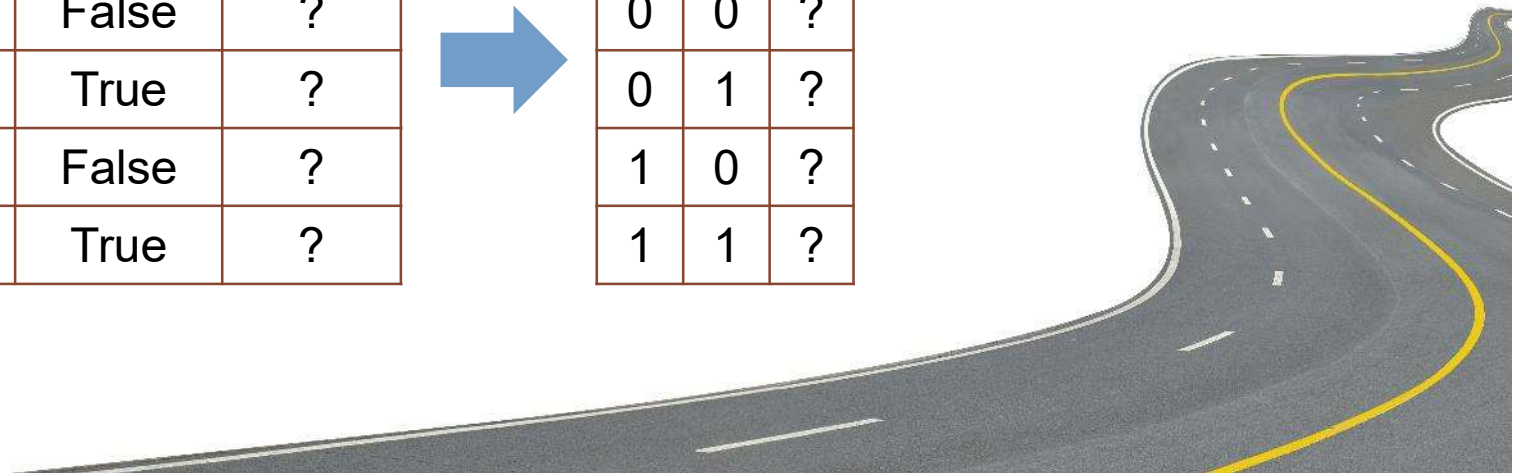


# Boolean function – OR

Answers

- IF lane1Open OR lane2Open
  - If lane one is open OR lane 2 is open then you can drive down the road
  - What is P?

lane1 Open	Lane2 Open	P
False	False	False
False	True	True
True	False	True
True	True	True

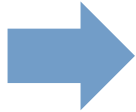

A	B	P
0	0	0
0	1	1
1	0	1
1	1	1

# Boolean function – NOT

- IF the input is **True** then the output is **False**
- IF the input is **False** then the output is **True**

Input A	Output P = NOT A
False	True
True	False

# More logic

Which of the following statements are **True**?

- $(4 > 3) \text{ AND } (5 > 7)$
- $(2 < 8) \text{ OR } (8 > 10)$
- $\text{NOT } (5 * 7 > 30)$
- $((7 \text{ DIV } 3) \geq 2) \text{ OR } ((7 \text{ DIV } 3) < 2)$
- $((12 \text{ MOD } 5) < 2) \text{ AND } ((12 \text{ MOD } 5) == 2)$ 
  - DIV gives the integer division (the result of division without any fractional component)
  - MOD gives the remainder after a division



# More logic

Answers


Which of the following statements are **True**?

- $(4 > 3) \text{ AND } (5 > 7)$  **False**
- $(2 < 8) \text{ OR } (8 > 10)$  **True**
- $\text{NOT } (5 * 7 > 30)$  **False**
- $((7 \text{ DIV } 3) \geq 2) \text{ OR } ((7 \text{ DIV } 3) < 2)$  **True**
- $((12 \text{ MOD } 5) < 2) \text{ AND } ((12 \text{ MOD } 5) == 2)$  **False**


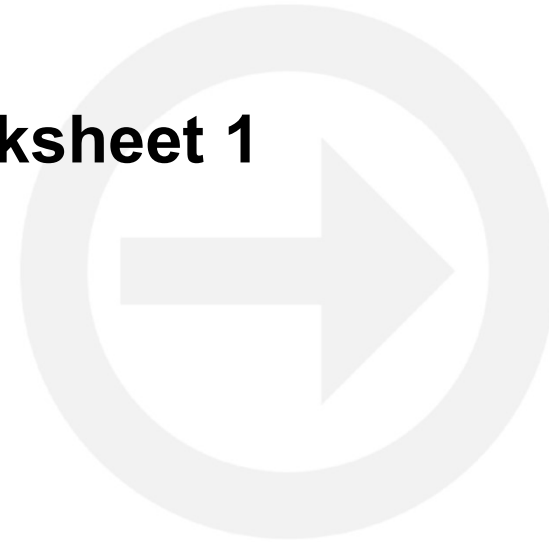
# Worksheet 1

- Now complete **Task 1** on **Worksheet 1**




# From truth tables to logic gates

- Physical computer circuits are built using logic gates
- The first three fundamental gates used to build circuits are:
  - AND gate
  - OR gate
  - NOT gate
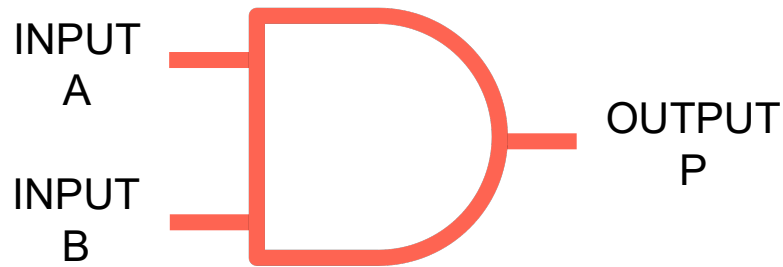
# Binary logic – AND gate

- If both inputs are 1 (True) then the output is 1 (True)
- Otherwise the output is 0 (False)



Logic statement:  $P = A \text{ AND } B$

Logic Diagram


A	B	P
0	0	?
0	1	?
1	0	?
1	1	?

Truth Table
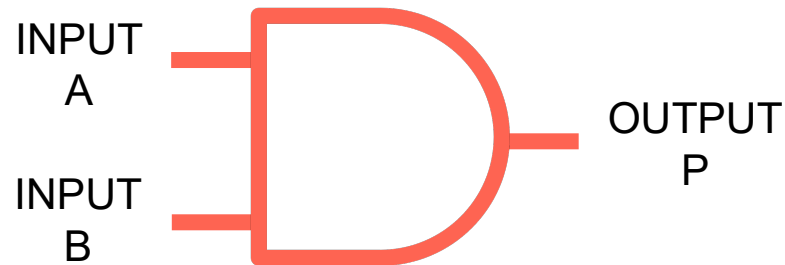
# Binary logic – AND gate

Answers

- If both inputs are 1 (True) then the output is 1 (True)
- Otherwise the output is 0 (False)



Logic statement:  $P = A \text{ AND } B$


Logic Diagram

A	B	P
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table
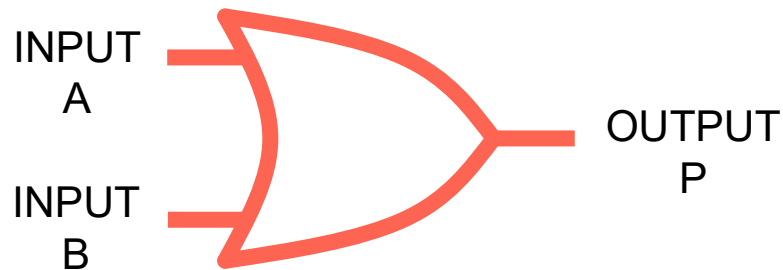
# Binary logic – OR gate

- If either input is 1 (True) then the output is 1 (True)
- Otherwise the output is 0 (False)



Logic statement:  $P = A \text{ OR } B$

Logic Diagram


A	B	P
0	0	?
0	1	?
1	0	?
1	1	?

Truth Table
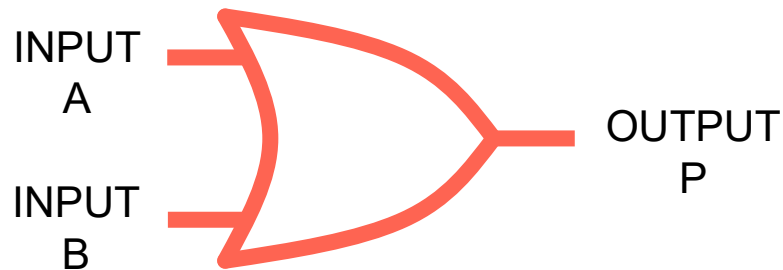
# Binary logic – OR gate

Answers

- If either input is 1 (True) then the output is 1 (True)
- Otherwise the output is 0 (False)



Logic statement:  $P = A \text{ OR } B$


Logic Diagram

A	B	P
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table
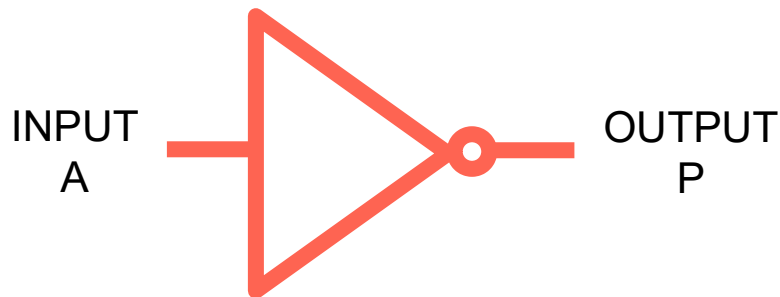
# Binary logic – NOT gate

- If 0 is input it outputs 1 (True)
- If 1 is input it outputs 0 (False)



Logic statement:  $P = \text{NOT } A$

Logic Diagram

A	P
0	?
1	?


Truth Table


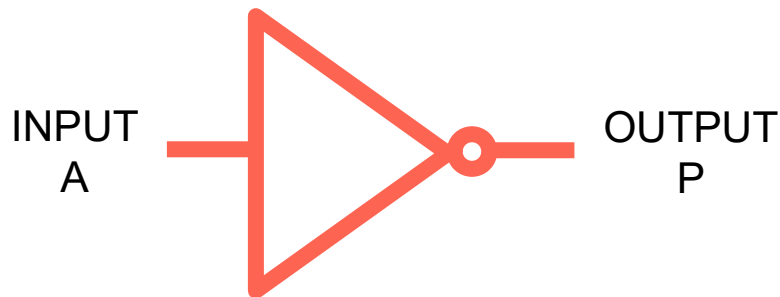
# Binary logic – NOT gate

Answers

- If 0 is input it outputs 1 (True)
- If 1 is input it outputs 0 (False)



Logic statement:  $P = \text{NOT } A$


Logic Diagram

A	P
0	1
1	0

Truth Table

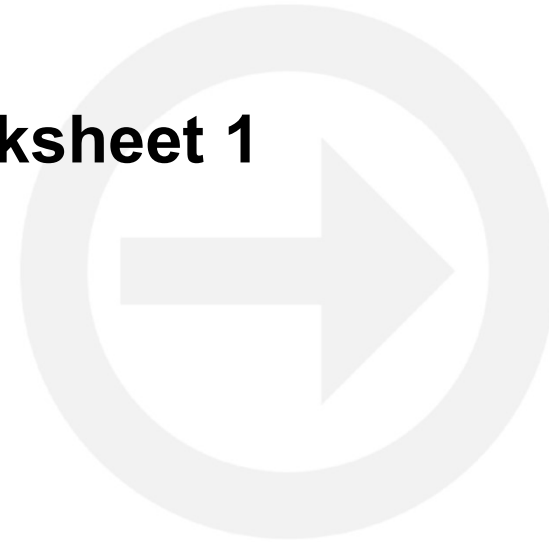
# Worksheet 1

- Now complete **Task 2** on **Worksheet 1**


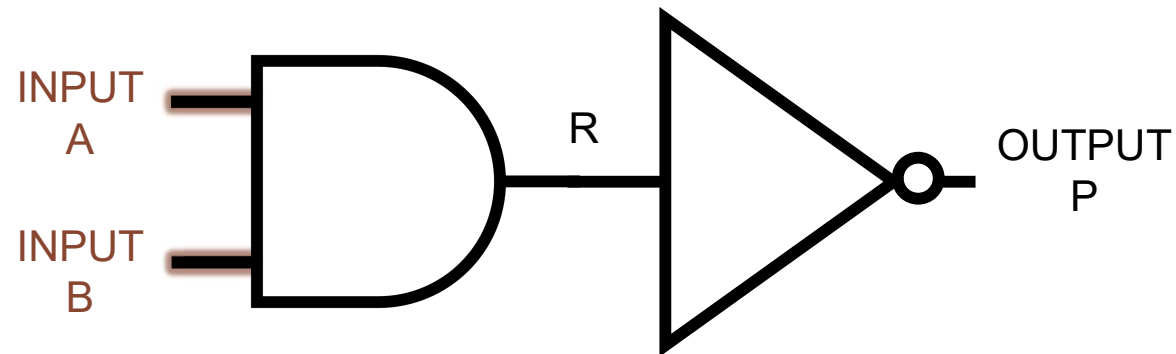
# Combining logic gates

- We can combine logic gates together to make more complex circuits




A	B	R = A AND B	P = NOT R
0	0		
0	1		
1	0		
1	1		

**Logic statement:**  
 **$P = \text{NOT}(A \text{ AND } B)$**
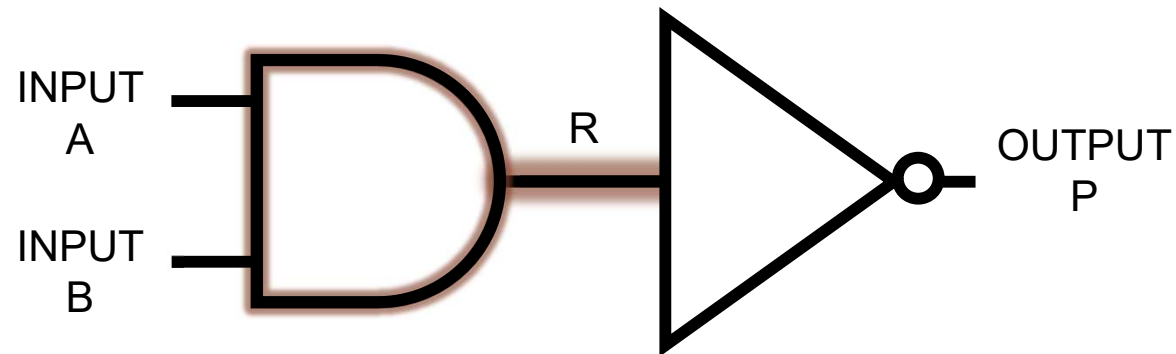
# Combining logic gates

- We can combine logic gates together to make more complex circuits




A	B	R = A AND B	P = NOT R
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

**Logic statement:**  
 **$P = \text{NOT } (A \text{ AND } B)$**
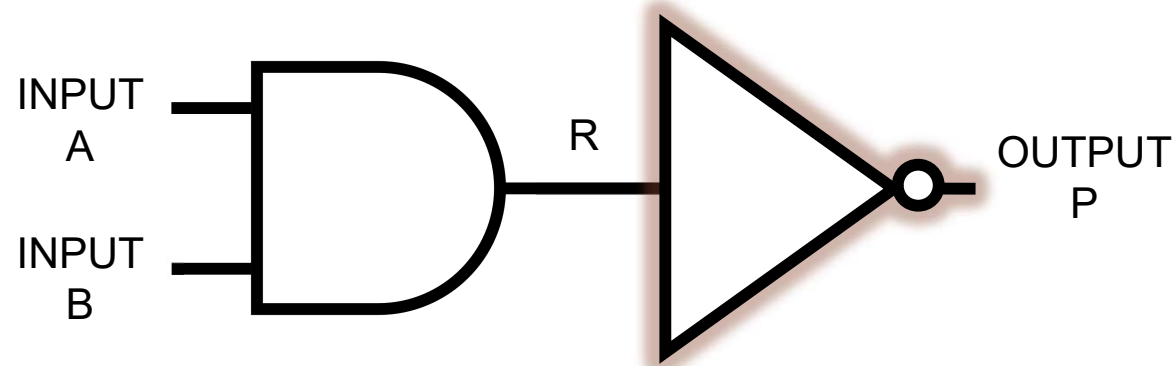
# Combining logic gates

- We can combine logic gates together to make more complex circuits



A	B	R = A AND B	P = NOT R
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

**Logic statement:**  
 **$P = \text{NOT } (A \text{ AND } B)$**

# Modelling real life – security lighting

- What would the circuit diagram for this situation look like?
  - The security light must come on if it senses movement AND it is night time, OR if someone presses a manual override switch



# Modelling real life

Answers

Sensor detects  
movement = TRUE



AND

Night time  
= TRUE



OR

Manual override  
Button = TRUE



=


Security  
Light On



Sensor detects  
Movement (S)

Night time (N)


Manual override  
Button (B)

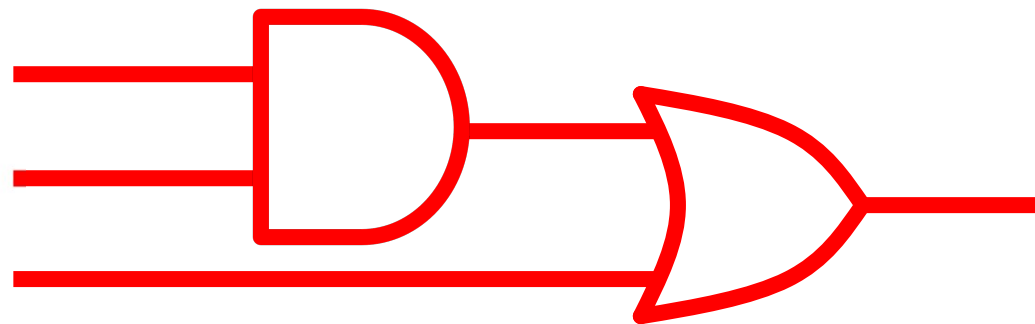

Security  
Light



# The truth table

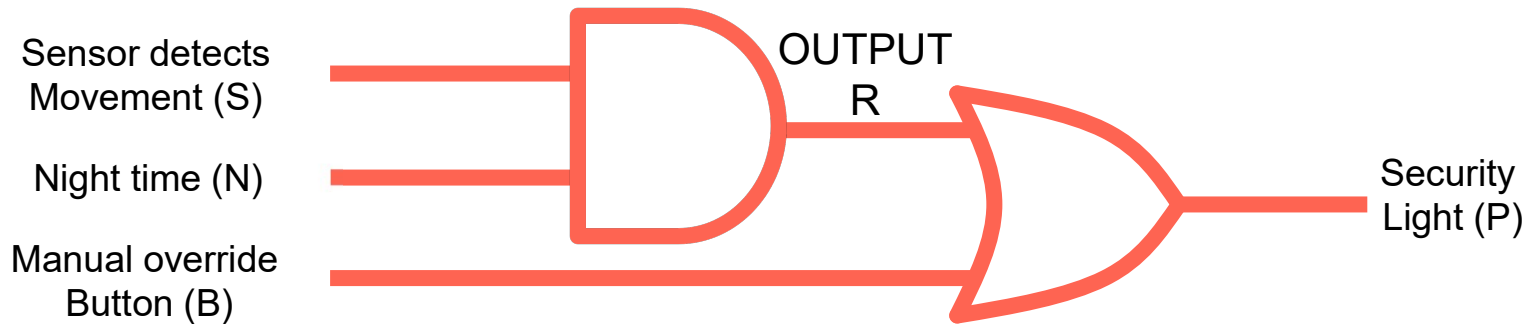


S	N	B	R = S AND N	P = R OR B

**Logic statement:**  
 $P = (S \text{ AND } N) \text{ OR } B$




# The truth table

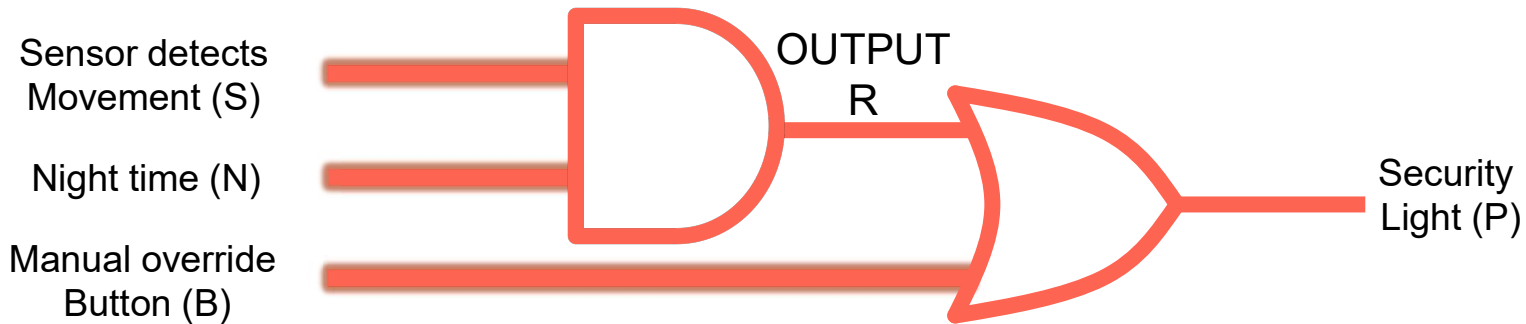

S	N	B	R = S AND N	P = R OR B
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

**Logic statement:**  
 $P = (S \text{ AND } N) \text{ OR } B$


# The truth table

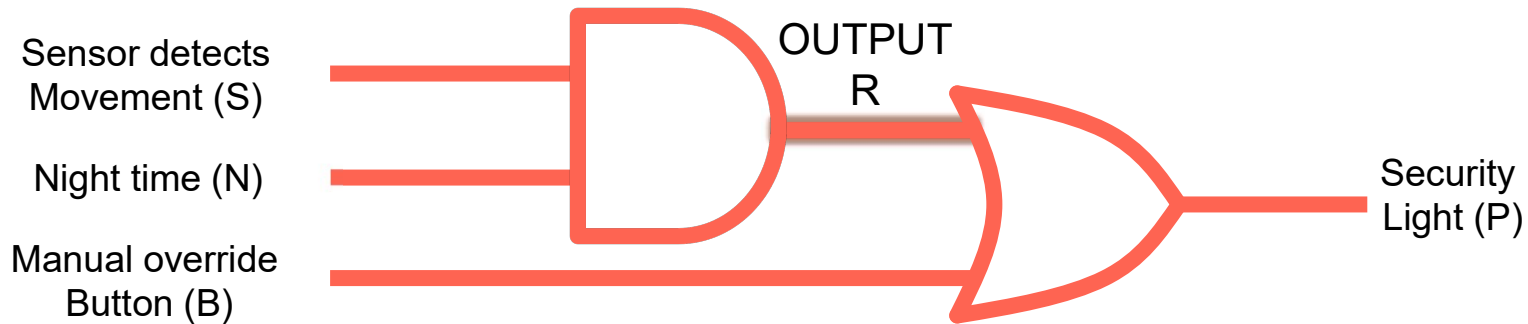

S	N	B	R = S AND N	P = R OR B
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	0	
1	1	0	1	
1	1	1	1	

**Logic statement:**  
 $P = (S \text{ AND } N) \text{ OR } B$

# The truth table

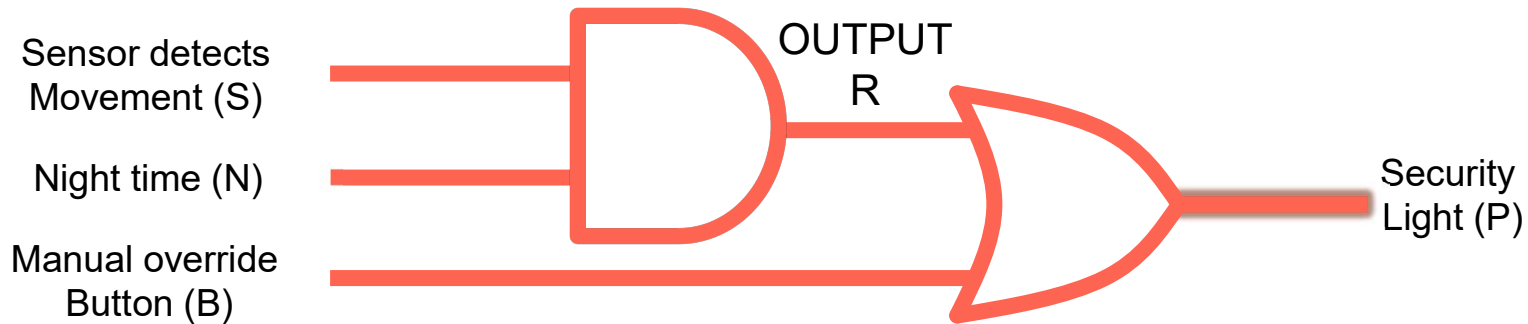


S	N	B	R = S AND N	P = R OR B
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	1
1	1	1	1	1

**Logic statement:**  
 $P = (S \text{ AND } N) \text{ OR } B$

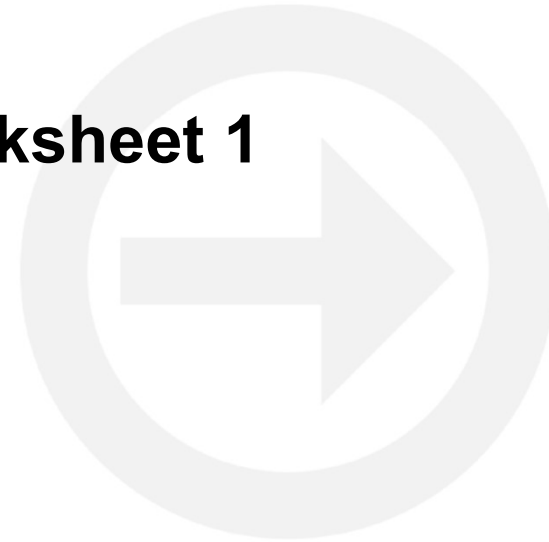
# Worksheet 1

- Now complete **Task 3** on **Worksheet 1**


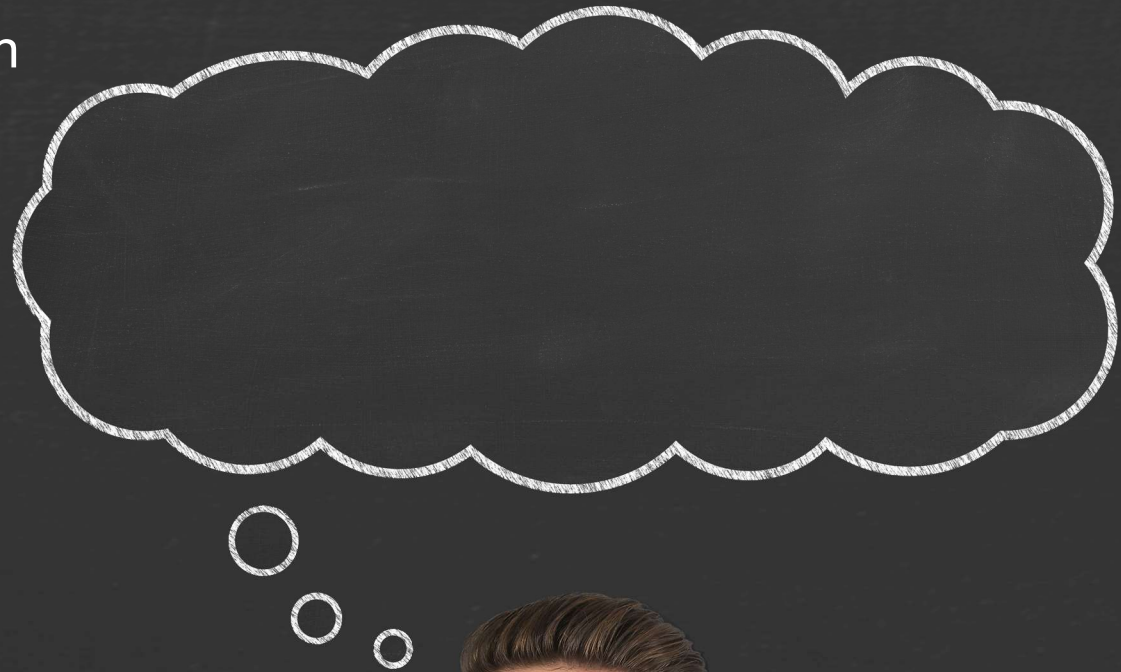
# Plenary

- Answer the following questions with a partner:
  1. What are the three basic logic gates?
  2. What are the symbols for each of the logic gates?
  3. Explain what each logic gate does
  4. What is a truth table?



# Plenary

## Answers

1. What are the three basic logic gates?

- AND, OR, NOT

2. What are the symbols for each of the logic gates?

- AND  OR  NOT 

3. Explain what each logic gate does

- AND – Both inputs must be True for output to be True
- OR – At least one input must be True for output to be True
- NOT – The output is opposite to the input

4. What is a truth table?

- It shows all possible combinations of inputs and the outputs they create



## Copyright

© 2020 PG Online Limited

The contents of this unit are protected by copyright.

This unit and all the worksheets, PowerPoint presentations, teaching guides and other associated files distributed with it are supplied to you by PG Online Limited under licence and may be used and copied by you only in accordance with the terms of the licence. Except as expressly permitted by the licence, no part of the materials distributed with this unit may be used, reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic or otherwise, without the prior written permission of PG Online Limited.

## Licence agreement

This is a legal agreement between you, the end user, and PG Online Limited. This unit and all the worksheets, PowerPoint presentations, teaching guides and other associated files distributed with it is licensed, not sold, to you by PG Online Limited for use under the terms of the licence.

The materials distributed with this unit may be freely copied and used by members of a single institution on a single site only. You are not permitted to share in any way any of the materials or part of the materials with any third party, including users on another site or individuals who are members of a separate institution. You acknowledge that the materials must remain with you, the licencing institution, and no part of the materials may be transferred to another institution. You also agree not to procure, authorise, encourage, facilitate or enable any third party to reproduce these materials in whole or in part without the prior permission of PG Online Limited.