

2.1 Current, Potential Difference & Resistance

Question Paper


Course	AQA GCSE Physics
Section	2. Electricity
Topic	2.1 Current, Potential Difference & Resistance
Difficulty	Medium

Time allowed: 70
Score: /56
Percentage: /100

Question 1a

Figure 1 shows a graph of current against potential difference for a circuit component

Figure 1

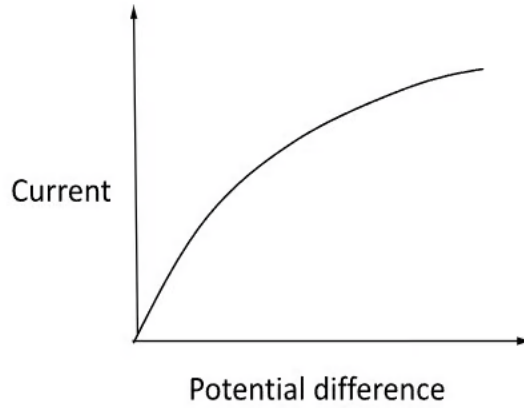

- (a)
What is the name of the component?

[1 mark]

[1 mark]

Question 1b

- (b)
Explain how the resistance of the component changes as the potential difference across it increases.

[3 marks]

[3 marks]

Question 1c

(c)
LED lamps are considerably more energy efficient than the old filament bulbs that can be found in many houses.
What does 'more energy efficient' mean?


[1 mark]

[1 mark]

Question 1d

(d)
It is useful to be able to detect temperature, and then to turn on a heater when it gets cold.
A thermistor is a component that allows us to do this.
Part of a control circuit for doing this is shown in **Figure 2**.

Figure 2

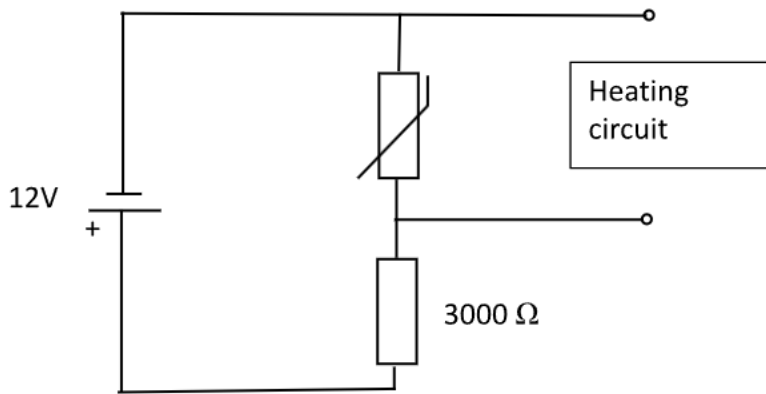

The temperature decreases.

What happens to the resistance of the thermistor, the current through the thermistor and the potential difference across it?

[3 marks]

Resistance _____ Ω

Potential difference _____

Current _____

[3 marks]

Question 1e

(e)

What is the resistance of the thermistor when the potential difference across it is 3 V?

Give a reason for your answer.

Explain your answer.

[2 marks]

[2 marks]

Question 1f

(f)

Calculate the current through the thermistor when the resistance of the thermistor is 5000 Ω .

Give your answer to 2 significant figures.


[4 marks]

[4 marks]

Question 2a

The diagram in **Figure 3** below shows a sensing circuit which is used to control a set of automatic lights.

Figure 3

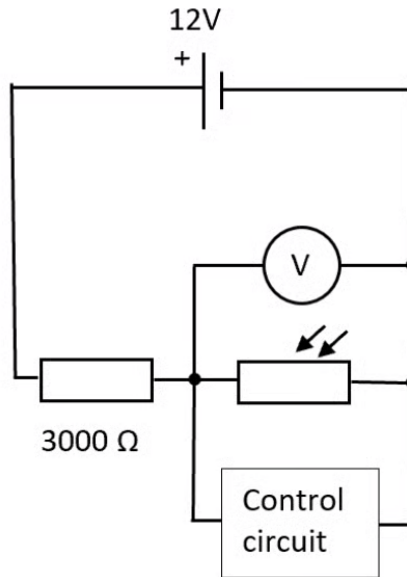

- (a) What quantity is measured by the voltmeter?

[1 mark]

[1 mark]

Question 2b

- (b) Add an ammeter to the diagram which could measure the current through the LDR.

[1 mark]

[1 mark]

Question 2c

- (c) When the potential difference across the LDR is 6.4 V, the current in the circuit is 4.8 mA.

Calculate the resistance of the LDR.

[3 marks]

[3 marks]

Question 2d

- (d) Explain why the potential difference across the thermistor changes as the temperature in the house decreases.

[2 marks]

[2 marks]

Question 2e

- (e) The circuit is left to run for 10 minutes. Calculate the charge that flows in 10 minutes when the current in the circuit is 4.8 mA

[3 marks]


[3 marks]

Question 3a


A student investigated how current varies with potential difference for two different resistors.

Her results are shown in **Figure 4** below.

Figure 4

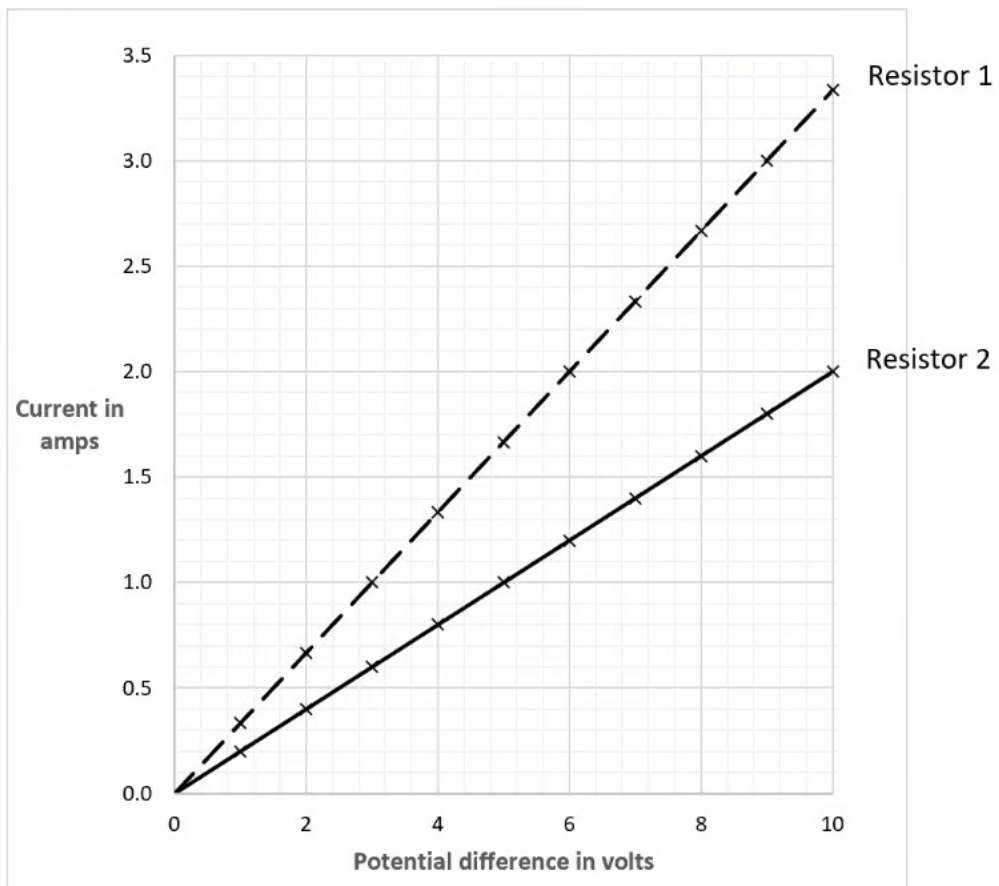

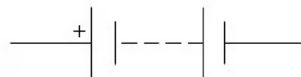- (a) Complete the circuit diagram for the circuit that the student could have used to obtain the results shown in the figure above.



[3 marks]

[3 marks]

Question 3b

- (b) Resistor 2 has the **higher** resistance.

Explain how this is shown by the graph above in **Figure 4**.

[2 marks]

[2 marks]

Question 3c

- (c) Both resistors behave like ohmic conductors for the full range of potential differences used in this investigation.

Explain what an ohmic conductor is.

[2 marks]

[2 marks]

Question 3d

- (d) Use the graph above in **Figure 4** to calculate the resistance of both resistor 1 and resistor 2.

[2 marks]

[2 marks]

Question 3e

- (e) Resistor 1 and resistor 2 are placed in series with each other.

Calculate the Total resistance of this combination.

[1 mark]


[1 mark]

Question 4a

Thermistors can be used as digital thermometers if their resistance is known at a variety of different temperatures.

The apparatus required to obtain the data necessary to carry out this calibration is shown in **Figure 5** below.

Figure 5

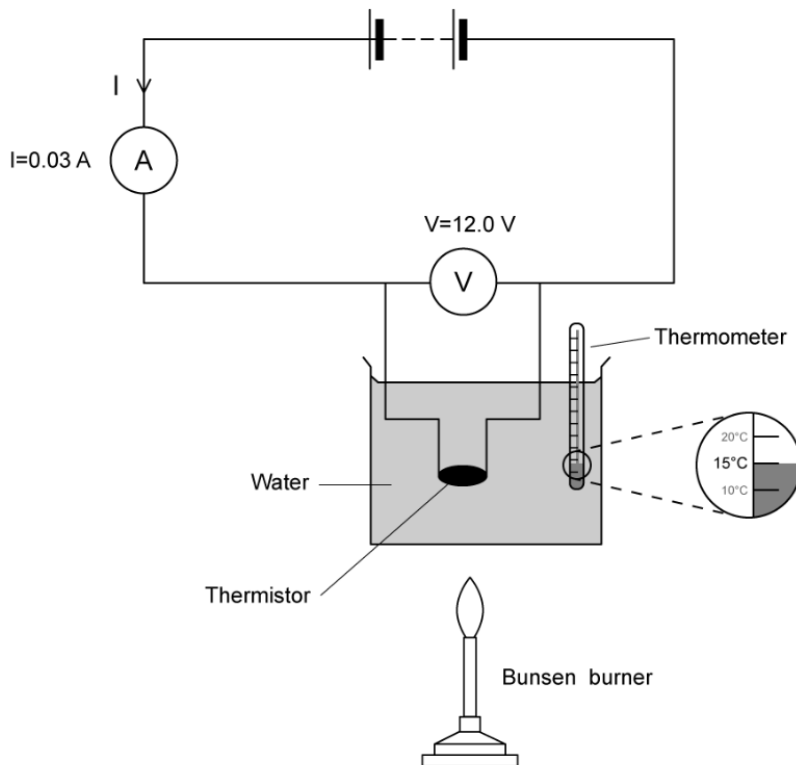

(a) In the space below, draw the circuit symbol for a thermistor.

[1 mark]

[1 mark]

Question 4b

- (b) Calculate the resistance of the thermistor at 15°C , using the data from **Figure 5**.

[2 marks]


[2 marks]

Question 4c

- (c) Complete the sketch graph in **Figure 6** below to show how the resistance of a thermistor changes between the temperatures of 15°C and 100°C .

[1 mark]

Figure 6

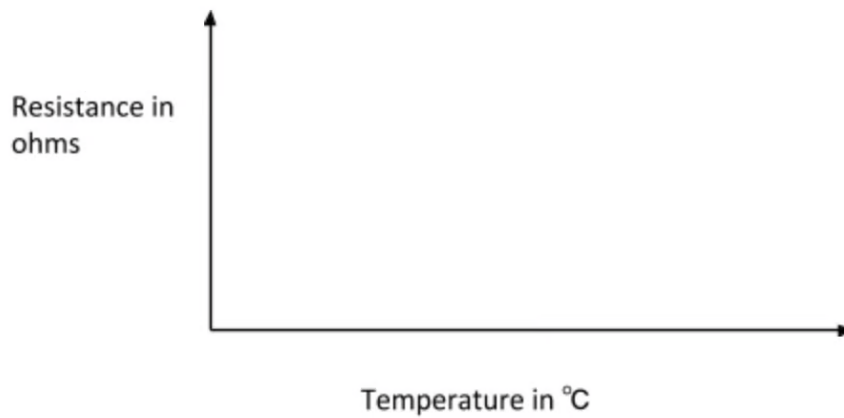

[1 mark]

Question 4d

- (d) Give an example of a device that could include a thermistor

[1 mark]

[1 mark]

Question 4e

- (e) Ammeters, which are used in circuits have very low resistances.

Why is it important that ammeters have a very low resistance?

[1 mark]

[1 mark]

Question 4f

- (f) A student plans to change the experiment in **Figure 6** to investigate how the resistance of an LDR changes with the intensity of light shone on it.

Once change the student makes is to replace the thermistor with an LDR.

Suggest **two** further changes the student should make to the apparatus.

[2 marks]

[2 marks]

Question 5a

Some students are investigating the I-V characteristics of a fixed resistor.

(a)

The students are given the following equipment:

- An ammeter
- A voltmeter
- A variable resistor
- Fixed resistors of $100\ \Omega$, $200\ \Omega$, $400\ \Omega$ and $500\ \Omega$
- A power pack
- Wires

Draw a circuit using the equipment from the list that would enable the students to gather valid data.

[4 marks]

[4 marks]

Question 5b

(b)

Describe a method that would allow the students to obtain valid results.

[5 marks]


[5 marks]

Question 5c

(c)

The students plotted their data and produced the graph shown in **Figure 1**.

Figure 1

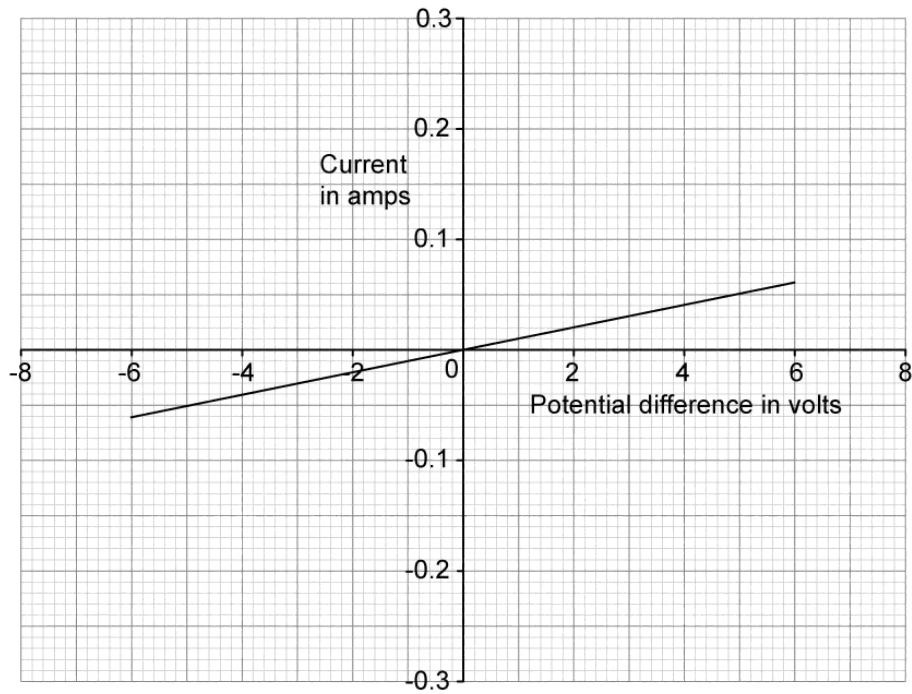

Write down an expression for the gradient of the graph in terms of **resistance**.

[1 mark]

[1 mark]

Question 5d

(d)

Use the graph to determine the resistance of the fixed resistor used by the students.

[4 marks]

Resistance = Ω

[4 marks]