

# 2.2 Series & Parallel Circuits

## Question Paper


Course	AQA GCSE Physics
Section	2. Electricity
Topic	2.2 Series & Parallel Circuits
Difficulty	Medium

**Time allowed:** 50  
**Score:** /38  
**Percentage:** /100

**Question 1a**

- (a) The circuit in **Figure 1** shows how an LDR can be used to turn on a circuit when it gets dark.

**Figure 1**

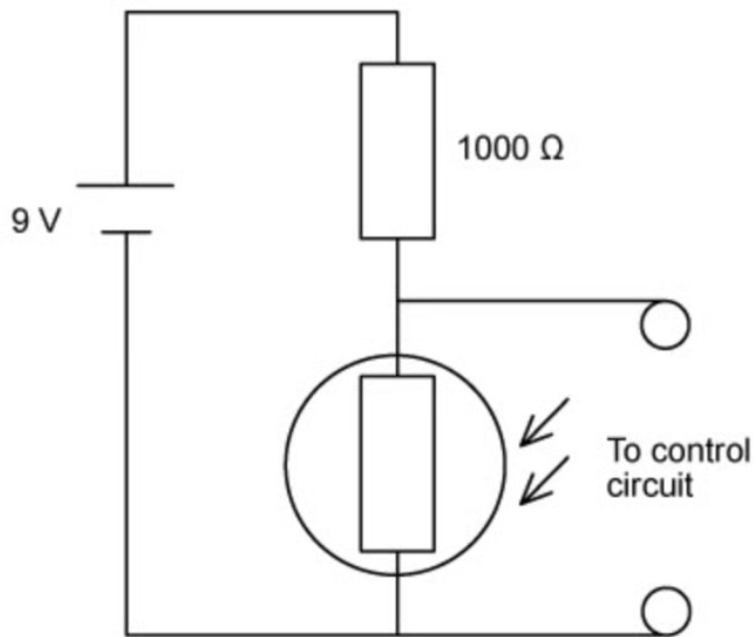

If the light intensity decreases, what happens to the current and the potential difference across the LDR?

**[2 marks]**

[2 marks]

**Question 1b**

(b) When the potential difference across the LDR is 3 V, what is its resistance?

Explain your answer.

**[2 marks]**

[2 marks]

**Question 1c**

(c) When the light gets dimmer, the resistance of the LDR becomes  $1000 \Omega$ .

Calculate the current through the LDR when its resistance is  $1000 \Omega$ .

Give your answer to **3 significant figures**.

**[4 marks]**

[4 marks]

**Question 2a**

A student has four resistors.

Each resistor has a resistance of  $100 \Omega$ .

- (a) Explain how the resistors should be connected so that the total resistance is as low as possible.


**[2 marks]**

[2 marks]

**Question 2b**

- (b) The four resistors are connected in series with a 3 V cell, as shown in **Figure 2** below.

**Figure 2**

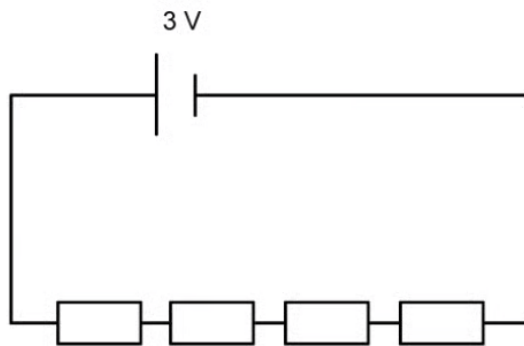

Calculate the current that flows through the cell.

Give your answer to **3 significant figures**.

**[3 marks]**

[3 marks]

**Question 2c**

- (c) Add an ammeter to **Figure 2** which would allow the current through the cell to be measured.


**[2 marks]**

[2 marks]

Question 3a

A student set up the circuit in **Figure 3** below.

**Figure 3**

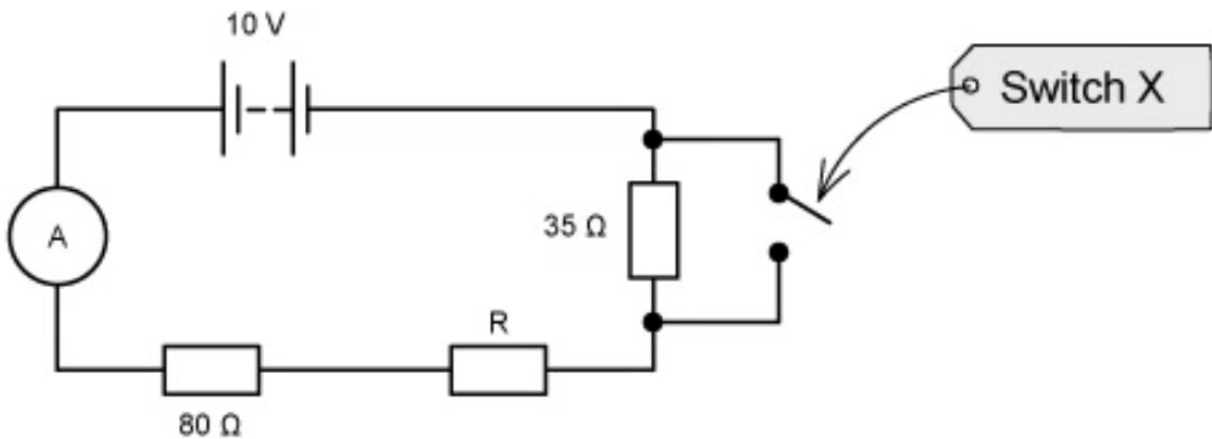

(a) The ammeter displays a reading of 0.075 A.

Calculate the potential difference across the 80 Ω resistor.

[2 marks]

[2 marks]

### Question 3b

(b) Calculate the resistance of resistor **R** in **Figure 3**.

**[3 marks]**

[3 marks]

### Question 3c

(c) Switch **X** is closed.

State what will happen to the total resistance of the circuit **and** the current through the circuit.

**[2 marks]**

[2 marks]

### Question 3d

(d) Calculate the new current through the circuit.


**[3 marks]**

[3 marks]

**Question 4a**

The circuit diagram in **Figure 8** shows two resistors connected in parallel.

**Figure 8**

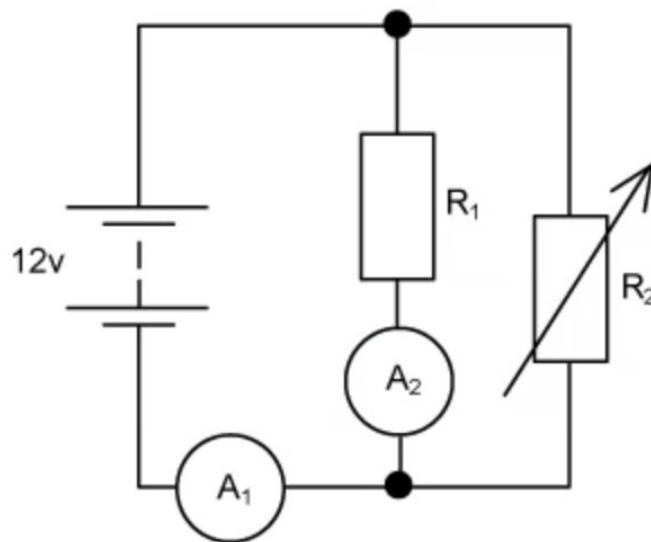

Reading on ammeter  $A_1 = 3 \text{ A}$

Reading on ammeter  $A_2 = 1 \text{ A}$

Using the circuit diagram in **Figure 8**, answer the questions below:

(a) What is the potential difference across resistor  $R_1$ ?

**[1 mark]**

[1 mark]



**Question 4b**

(b) Calculate the resistance of resistor  $R_1$ .

**[2 marks]**

[2 marks]

**Question 4c**

(c) What is the current flowing through the variable resistor  $R_2$ ?

**[1 mark]**

[1 mark]

**Question 4d**

(d) Calculate the resistance of the variable resistor  $R_2$ .

**[1 mark]**

[1 mark]

**Question 4e**

(e) The resistance of the variable resistor  $R_2$  is increased.

What would happen to:

- The current through  $R_2$
- The potential difference across  $R_2$
- The current through the battery?

Tick (✓) **three** boxes

**[3 marks]**

	<b>Increase</b>	<b>Stay the same</b>	<b>Decrease</b>
<b>Current through <math>R_2</math></b>			
<b>potential difference across <math>R_2</math></b>			
<b>current through the battery</b>			


**[3 marks]**

**Question 5a**

**Figure 4** below shows how two resistors can be connected in series or in parallel to a 12 V cell.

The resistors are identical.

**Figure 4**

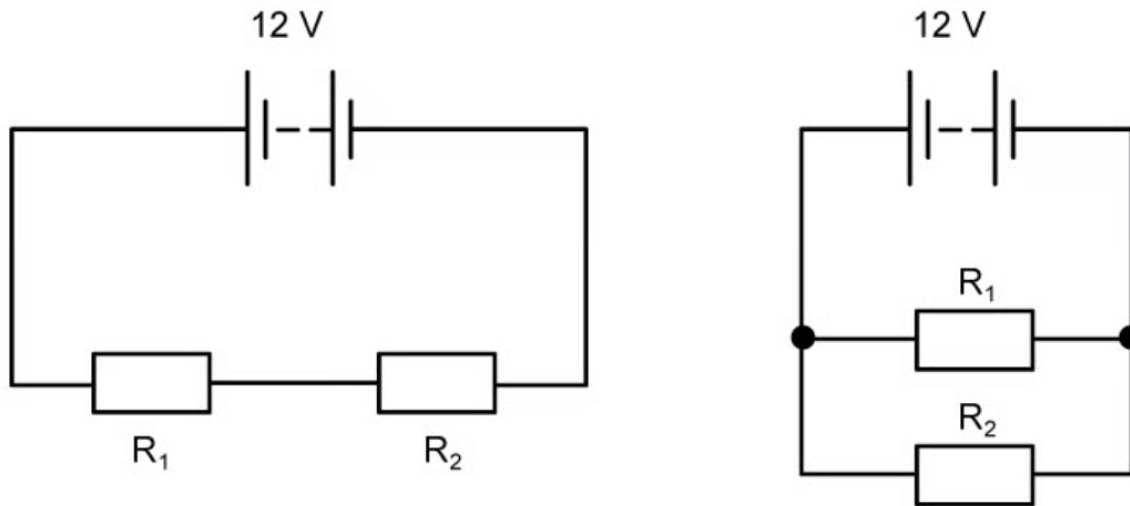

(a) Calculate the potential difference across each resistor when the lamps are connected in series and in parallel.

**[2 marks]**

[2 marks]

**Question 5b**

(b) Give one disadvantage of connecting the lamps in series rather than in parallel.


**[1 mark]**

[1 mark]

Question 5c

Figure 5 shows how an ammeter can be used to measure the current flowing through the battery for the same circuit.

Figure 5

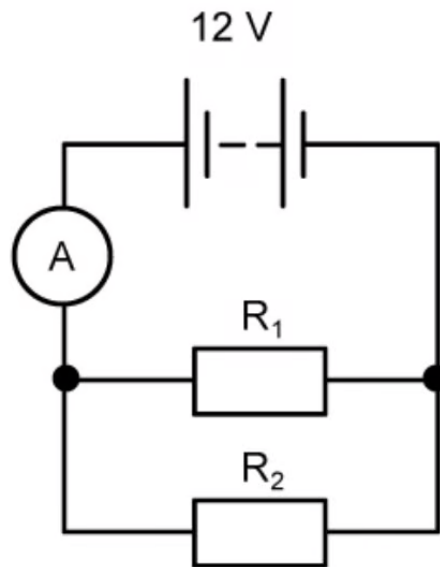

The reading on the ammeter is 1.6 A.

(c) Add an ammeter to **Figure 5** to show how to measure the current through resistor  $R_2$ .

[1 mark]

[1 mark]

Question 5d

(d) The resistors are identical.

State the current through resistor  $R_2$ .

[1 mark]

[1 mark]